

Digital Design and Synthesis

INTRODUCTION

The advances in digital design owe its progress to 3 factors. First the acceleration at which the CMOS technology has advanced in last few decades and the way that information has been stored and processed. Secondly, the driver for digital design has been the ability to treat all kinds of media as digital data that is stored, processed and manipulated and finally combining and storing all sorts of information and data in a single document and the third parameter is, the transmission in high speed over long distances. These concepts increased the requirement for digital design and ways to optimise its performance.

 


Fig.1 Design description levels

Digital system and its design can be described in three domains namely: ***Behavioural, Structural and Physical*** domains as shown in Fig.1. In each domain, the level of description and decision to be taken and the complexity are different.

The behavioural description is usually language based and can be pure algorithmic or signal flow graphs or even a transfer function and more likely a HDL Code. For example a multiplier can be described by $A * B = C$. At the behavioural level we may decide in using a serial or a parallel multiplier. So trade offs for speed, cost, chip area, power consumption etc. is made in this level. Many high level details are decided upon while the lower level details are compromised. Important design decisions such as what algorithm to be used for the system at hand are made at this level. It is important to know that the reward for optimization at this level is many folds of that of other levels as shown in Fig. 2. The digital designer starts the design at the conceptual level working with high level behavioural blocks and proceeds to design of major functional blocks that supports a given design specification. In order to manage complexity, the overall design may be partitioned and each partition dealt with separately using detailed structural constructs. In any case major decisions regarding algorithms, functional partitioning, structural partitioning and data transmission methods are made at this level while for each individual item optimising the speed, power consumption, area, and cost are identified. The benefit to the designer is that it provides a fast and accurate way to verify whether the concept is correct and design specification can be met and also provides means by which a compromise is reached between several objectives by “WHAT IF ANALYSIS”.

The behavioural analysis is used usually for “PROOF OF CONCEPT”.

Optimization Levels		
Level	Transformation	Expected Power Saving
Algorithmic	Algorithm selection	Orders of magnitude
Behavioural	Concurrency	Several times
Register Transfer Level	Structural transformations	~10 - 15%
	Clock control	~10 - 90%
Data/signal encoding		~20%
Technology independent	Extraction/decomposition	~15%
Technology dependant	Technology mapping	~20%
	Gate sizing	~20%
Layout	Placement	20%

Fig-2

The behavioural model is usually converted to RTL level in HDL or block diagram usually manually. At the structural level, we are dealing with data paths, practical logic blocks and their interconnection. We may want to decide upon Dynamic logic or Static logic, Serial or Parallel input registers, what kind of adder to be used, what kind of multiplier will meet our speed and area, what is our clocking strategy etc. Our project for this course this year will be based on Structural level, where you would design and code a multiplier in VHDL at structural level and then synthesise it to an FPGA. At the Structural level we use the EDA tools fully. At this level, The synthesis tools convert the blocks to gate level netlist and the logic synthesis tools optimize logic level design and the timing tools verify operations in terms of spec. requirement of timing, area and power.

At the physical level, we will try to design and implement the circuit on chip. (COEN 6511) where our variables will be at silicon level. At this level the netlist is input to the EDA tools such as place and route which produces a layout, The layout is extracted and fed again for verification through an iterative process. Once a final satisfaction with the spec is achieved the layout is ready for download for fabrication. For example, how the chip layout is arranged, where the pads will be located, and how the Vdd and Vss are distributed and how the boards are arranged, where are the components placed etc.

The Y chart of Fig. 1 shows that one can make a de-composition and a transition from behavioural level to structural level. This can be achieved manually or through silicon compilation. By the same token one can transform from structural level to gate and logic level by creating FFs, gates, and higher blocks such as registers, counters, all kinds of modules. Also one can transcend to the physical level to design the transistors that make up the gates and step further to the polygons of different materials that make the transistors. So one can start automatically or manually to transcend from behavioural to the physical level. Silicon compilers do exist that accept behavioural level description and proceed to the physical chip, or chip layout. In all cases HDL language ie VHDL/ Verilog or others high languages is a good starting point to describe the system at hand.

Generalizing then, logical synthesis is a structural form where the physical synthesis leads to the physical domain. Thus the design process includes the behavioural description followed by the decomposition of high level constructs into more precise functional units which are then mapped into the physical elements. The logical circuits that are commonly used are available as integrated circuits and are referred to as standard chips (in our design they are referred to as library cells). The advent of the very large scale integration (VLSI) has made the configuration on chip possible where a complete system can be designed synthesized and placed on a single chip.

As complexity of the chips is increased to billions of transistors on a chip, then design automation becomes necessary. Designers now can design large chips verify it, automatically place and route it, re-evaluate its characteristic, debug it and verify its final functions before downloading the bitmap file on the actual chip as Shown in Fig. 4. One must always that these tools depend on the input and the rule of garbage in garbage out still applies.

In general nowadays HDL is used extensively in digital design. The advantages are many including the design at the HDL level does not depend on any fabrication technology. Synthesis tools are available for converting the HDL to gate level netlist. The HDL is adaptable to new technologies, eliminating need for redesign. The verification tools at any step insure that all bugs are cleared and the design once goes to production is correct producing the exact requirement first time. Finally HDL, VHDL/Verilog/or higher level languages are becoming the

only method being used by designers. Currently the trend is to use structural design at the RTL level.

In general two basic types of methodologies can be defined namely top-down design and bottom-up design methodology. In top-down design methodology the top block is defined and then the sub-blocks necessary are identified in order to build a top level block. These are then further divided in progression into smaller units till we reach the leaf cells that cannot be divided further. The design is described in HDL and the HDL coding techniques will be applied to the design so that the design is modelled effectively and efficiently. Design errors that are obvious are checked through the preliminary synthesis of each HDL code and every block is verified before integrating it into a larger unit.

Design process

A design starts always with a specification. The specification describes what the circuit must do, but not how it is done. The specification is usually set by the customer who wants the final product. Once the designer knows what the circuit must do, she/he can begin to determine how it is done, for example, defining what are the inputs to the unit and the outputs that must be generated is a good first step.

The designer then starts with translating the design specification into behavioural description, then decomposing the high level constructs into functional units and finally, then mapping these units into physical elements as shown in Fig.3.

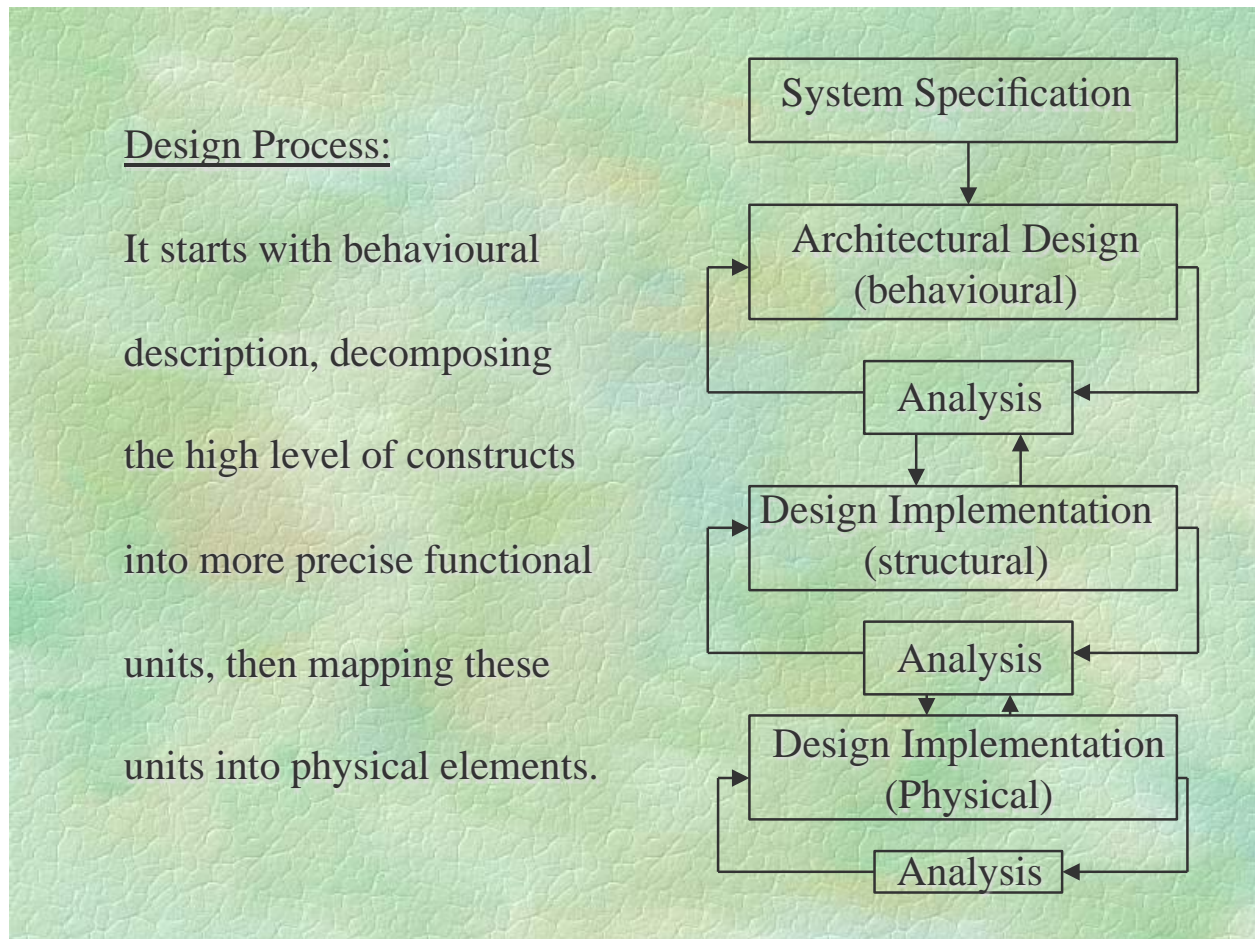


Fig. 3

A simple example of word specification from a customer may be as follows:

Required an 8 bit microprocessor, no cache, simple addressing mode, 8 internal registers, Instruction word 8 bits, 8 bit address bus multiplexed with data bus, 40 pin package, dual IP package and consuming less than 1 Watt. A simple diagram of the system is shown in Fig.4

The designer then gets to work as first step starting with block diagram, decomposes the overall system into components that are available in the library or to be designed. The block diagram below

 


Fig. 4

shows the behavioural description of the system. Now each item is broken down to smaller units, for example, the CPU maybe broken into adder, multiplier, floating point unit etc. Now each unit in turn is broken down further using identifiable structures. For example an eight bits multiplier can be designed as shown in Fig.5

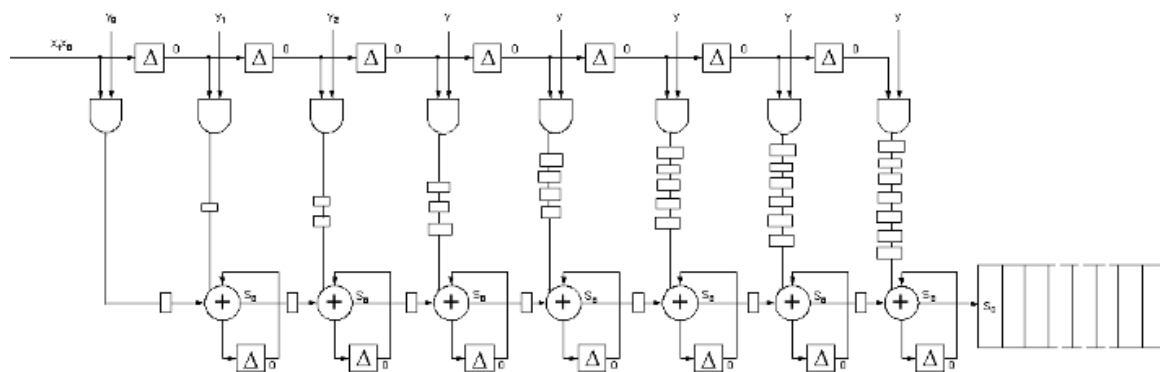


Fig. 5 An 8-bits multiplier

While each adder is designed as shown in Fig. 6 below:

 


Fig. 6 A 1-bit adder

This is a structured design where each unit is either designed specifically for this system or has been selected from the already available library.

When the design of all the individual units have been completed then the overall design is simulated and compared to the specification. When the design meets the spec, then it is targeted to a physical implementation.

As complexity of the chips is increased to billions of transistors on a chip, then design automation becomes necessary. Designers now can design large chips verify it, automatically place and route it, re-evaluate its characteristic, debug it and verify its final functions before downloading the bitmap file on the actual chip as Shown in Fig. 7

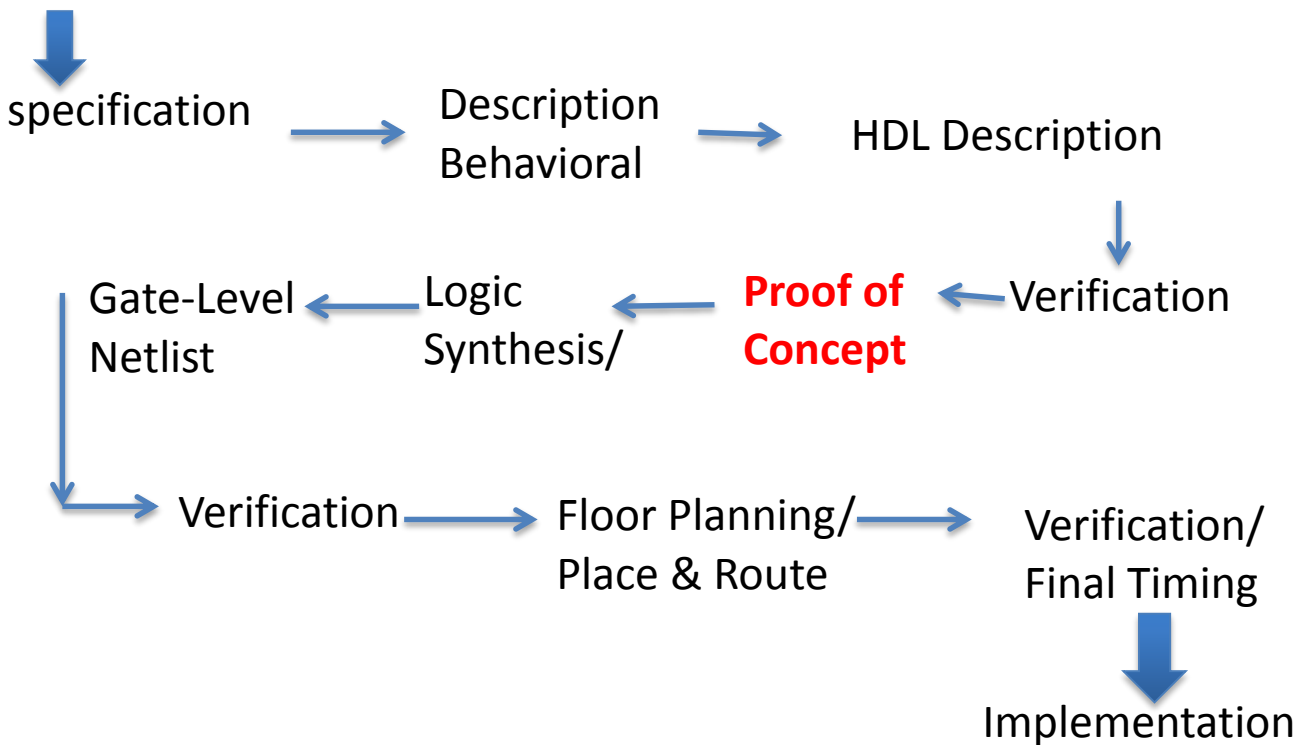


Fig. 7

Design Strategies

Any system is comprised of many individual units such as boards, chips, power supply, routing etc. The success of the overall system depends on how well it is optimized in terms of performance, and at the end of the product cycle, what is the revenue that the newly designed system generates. This in turn depends on how well each individual unit in the system was designed through all its design levels from the algorithm down to the devices. For example how well a chip is designed is measured by several criteria such as functionality, speed, power, size etc. On the other hand other factors also play an important part such as time to design, time to market and ease of testing. The final implementation has to conform to the original spec. or better. During the design there are many factors that can be traded for the good design, therefore the knowledge of all factors affecting the design and their interdependence are important.

Most designs nowadays are large and complex. A successful designer has to structure his design and use design automation tools available. In general a successful designer uses the following 4 principals to achieve his design effectively and quickly.


- 1) Hierarchy
- 2) Regularity
- 3) Modularity
- 4) Locality

Hierarchy,


This is an extremely useful strategy when you have a complex system. It is the process of divide and conquer. The overall system is repeatedly divided into subunits and in turn the subunits are divided further until no further division is possible or the subunits are available in the library. At this stage the design is more manageable since the smaller sub-modules can be designed easier.

The hierarchy can be in different domains in software or hardware modules. For example a VHDL entity module can be written or structurally designed in a hierarchical fashion. Parallel hierarchy is implemented in all domains. As an example a 4-bit adder can be designed by dividing the adder into 4 single bit adder, and an adder can be designed using 2 half adders and so on as shown below:



Regularity

 

Half adder

 

Full Adder

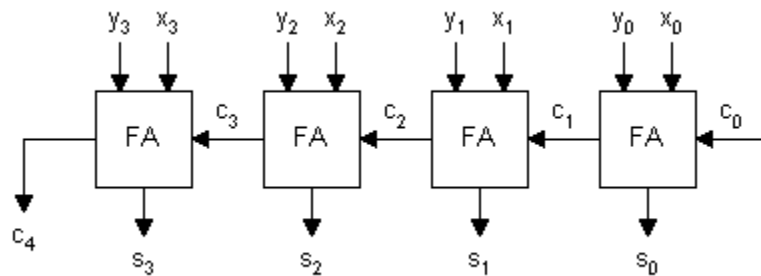 


4-bit Adder

Regularity

Although hierarchy can reduce complexity, however by applying regularity we can reduce complexity of the layout much further. This is because the method of simplify the work of the software that automates the design and in turn the design and implementation tasks are reduced. In this way, compact designs are obtained and finally verification of the design becomes simpler.

So at this stage we divide the hierarchy into smaller building blocks such that the small block can interlock in each other.

 For example an adder in a datapath design can be designed in a regular fashion in such a way that by concatenating the 1 bit of the adder n time an n bit adder is designed and implemented in layout directly.



Modularity,

This is designing a module such that it is interface-able to other modules in the system. This means taking into consideration all the electrical, mechanical and physical parameters into account. The unit is verified and perfectly characterized. This is performed such that the module is well defined and ready for integration into most designs and understood and can be used by other members of the team or design community to be placed in the library. It basically gives confidence to the average designer since the module is well characterized. In general modularity makes implementation of design principal easy,

Design principals: 1) Concatenation..... physical abutments

2) Iteration regular cells, arrays

3) Conditional selectionPLA, Transistor selection



Additional buffers for easy interfacing to other modules which have certain input and output characteristic


Locality

This is a strategy to ensure that only components or routs that are essential to the module stay in the module, or by other definition optimization of internal components is very important because this will be used in the overall system, any local parameter should be kept within the module and close to where it is used to reduce for example resistance or capacitance.

VHDL,

Due to complexity and speed of the design, designers have opted for design at higher level of abstraction. Designers follow functionality and let the Electronic Design Automation EDA, take care of the rest. The EDA tools are complete packages that take care of A to Z of the design translation, optimization and implementation.

Most designs nowadays are performed with the aid of high level languages such as VHDL or Verilog. This is so because these languages are design entry point, Specification language, as well as design simulation design verification tools. Thus it is a complete package by which the designer starts the specification to the end point by which the final VHDL code can be translated and synthesized into an FPGA or semi custom design. The design once described can be simulated and iterated through the design cycle until the final specification targeting a device for implementation is met. The following figure shows that most of the design, specification, simulation and verification can be done through VHDL.

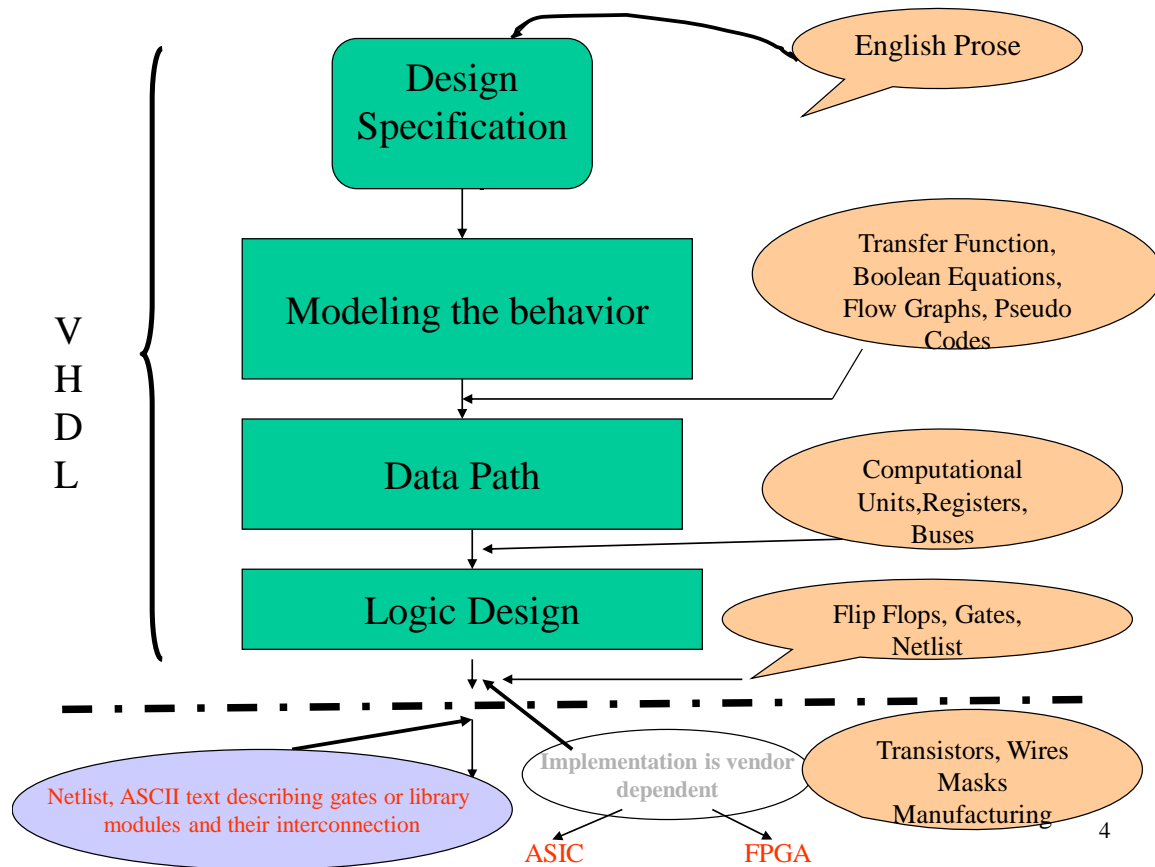

At each point the Synthesis tools will provide you a report to check the design and its performance in terms of Speed, Area and Power. At anytime also the designer can go back and change its design thus repeating the design process. The following diagrams show the output from the synthesis reports.

At the end of this course you will be doing your project. That requires design of a digital system, coding its behaviour at the structural level, writing the test bench, simulating the design and verifying its functionality as well as obtaining its performance.

Synthesis report

File	Edit	Search	Preferences	Shell	Macro	Windows	Help
I							
Report : fpga							
Design : SQUARER_8							
Version : V-2004.06-SP1							
Date : Tue Mar 7 21:00:01 2006							

Xilinx FPGA Design Statistics							

FG Function Generators:	203						
H Function Generators:	0						
Number of CLB cells:	232						
Number of Hard Macros and Other Cells:	0						
Number of CLBs in Other Cells:	0						
Total Number of CLBs:	232						
Number of Ports:	28						
Number of Clock Pads:	1						
Number of IOBs:	27						
Number of Flip Flops:	29						
Number of 3-State Buffers:	0						
Total Number of Cells:	260						

File

Edit

Search

Preferences

Shell

Macro

Windows

Help

Report : timing

-path full

-delay max

-max_paths 1

Design : SQUARER_8

Version : V-2004.06-SP1

Date : Tue Mar 7 21:00:01 2006

Operating Conditions: MCCOM Library: xprim_4010e-3

Wire Load Model: Model: top

Startpoint: SPREG0_1/SPREG0/DFP4/Q_INSIDE_reg

(rising edge-triggered flip-flop clocked by CLK)

Endpoint: DFP1/Q_INSIDE_reg

(rising edge-triggered flip-flop clocked by CLK)

Path Group: CLK

Path Type: max

Dev/Clust/Port Wire Load Model Library

SQUARER_8 4010e-3_avg xprim_4010e-3

Point Iner Path

clock CLK (rise edge) 0.00 0.00

clock network delay (ideal) 0.00 0.00

SPREG0_1/SPREG0/DFP4/Q_INSIDE_reg/K (clb_4000) 0.00 0.00 f

SPREG0_1/SPREG0/DFP4/Q_INSIDE_reg/Q0 (clb_4000) 4.50 4.50 f

SPREG0_1/SPREG0/DFP4/Q (DIFF_0) 0.00 4.50 f

SPREG0_1/SPREG0/2 (SP_REG_4_0) 0.00 4.50 f

SPREG0_1/2 (SP_REG_0) 0.00 4.50 f

UA/PAD (clb_4000) 8.50 13.00 f

MUX/S (MUX_2to1_5) 0.00 13.00 f

MUX/NOT1/A (NOT_2_37) 0.00 13.00 f

MUX/NOT1/U7/X (clb_4000) 3.15 16.15 f

MUX/NOT1/A_NOT (NOT_2_37) 0.00 16.15 f

MUX/AND2/B (AND_2_26) 0.00 16.15 f

File Edit Search Preferences Shell Macro Windows Help

CEABRIT_1/RCAL/FADD4/HADD2/HAND1/B (NAND_2_16) 0.00 66.05 f

CEABRIT_1/RCAL/FADD4/HADD2/HAND1/0/X (clb_4000) 3.15 69.20 f

CEABRIT_1/RCAL/FADD4/HADD2/HAND1/U7/X (clb_4000) 3.15 72.35 f

CEABRIT_1/RCAL/FADD4/HADD2/HAND1/0 (NAND_2_16) 0.00 72.35 f

CEABRIT_1/RCAL/FADD4/HADD2/NOT1/A (NOT_2_39) 0.00 72.35 f

CEABRIT_1/RCAL/FADD4/HADD2/NOT1/U7/X (clb_4000) 3.15 75.50 f

CEABRIT_1/RCAL/FADD4/HADD2/NOT1/A_NOT (NOT_2_39) 0.00 75.50 f

CEABRIT_1/RCAL/FADD4/HADD2/C (HADD2_16) 0.00 75.50 f

CEABRIT_1/RCAL/FADD4/0/B (OR_2_23) 0.00 75.50 f

CEABRIT_1/RCAL/FADD4/OR1/U7/X (clb_4000) 7.25 83.35 f

CEABRIT_1/RCAL/FADD4/OR1/B (OR_2_23) 0.00 83.35 f

CEABRIT_1/RCAL/FADD4/Cont (FADDER_0) 0.00 83.35 f

CEABRIT_1/RCAL/Cont (RCAL_4BIT_1) 0.00 83.35 f

CEABRIT_1/MUX/S (MUX_2to1_0) 0.00 83.35 f

CEABRIT_1/MUX/NOT1/A (NOT_2_0) 0.00 83.35 f

CEABRIT_1/MUX/NOT1/U7/X (clb_4000) 3.15 86.50 f

CEABRIT_1/MUX/NOT1/A_NOT (NOT_2_0) 0.00 86.50 f

CEABRIT_1/MUX/AND2/B (AND_2_16) 0.00 86.50 f

CEABRIT_1/MUX/AND2/U7/X (clb_4000) 3.15 89.65 f

CEABRIT_1/MUX/AND2/B (AND_2_16) 0.00 89.65 f

CEABRIT_1/MUX/OR1/B (OR_2_16) 0.00 89.65 f

CEABRIT_1/MUX/OR1/U7/X (clb_4000) 3.15 92.80 f

CEABRIT_1/MUX/OR1/2 (OR_2_0) 0.00 92.80 f

CEABRIT_1/MUX/2 (MUX_2to1_0) 0.00 92.80 f

CEABRIT_1/Cont (RCAL_4BIT_0) 0.00 92.80 f

DFP1/D (DIFF_0) 0.00 92.80 f

DFP1/Q_INSIDE_reg/C1 (clb_4000) 0.00 92.80 f

data arrival time 92.80

clock CLK (rise edge) 96.00 96.00

clock network delay (ideal) 0.00 96.00

clock uncertainty -0.05 95.95

DFP1/Q_INSIDE_reg/K (clb_4000) 0.00 95.95 f

library setup time -2.42 93.53

data required time 93.53

Timing Report

After Synthesis

Timing Report After Synthesis

Area report after Synthesis

```

File Edit Search Preferences Shell Macro Windows Help
I
*****
Report : area
Design : SQUARER_8
Version: V-2004.06-SP1
Date   : Tue Mar  7 21:00:01 2006
*****

Library(s) Used:

  xfpga_4000e-3 { File: /CMC/tools/xilinx_vM3.1i/synopsys/libraries/syn/xfpga_4000e-3.db)
  xprim_4010e-3 { File: /CMC/tools/xilinx_vM3.1i/synopsys/libraries/syn/xprim_4010e-3.db)

Number of ports:      28
Number of nets:       117
Number of cells:       46
Number of references:  20

Combinational area:    0.000000
Noncombinational area: 259.000000
Net Interconnect area: undefined {Wire load has zero net area)

Total cell area:       259.000000
Total area:            undefined

```

Power report after Synthesis

```

File Edit Search Preferences Shell Macro Windows Help
*****
Report : power
Design : SQUARER_8
Version: V-2004.06-SP1
Date   : Tue Mar  7 21:00:03 2006
*****

Library(s) Used:

  xfpga_4000e-3 { File: /CMC/tools/xilinx_vM3.1i/synopsys/libraries/syn/xfpga_4000e-3.db)
  xprim_4010e-3 { File: /CMC/tools/xilinx_vM3.1i/synopsys/libraries/syn/xprim_4010e-3.db)

Warning: The library cells used by your design are not characterized for internal power. {PWR-2

Operating Conditions: WCCOM Library: xprim_4010e-3
Wire Load Model Mode: top

Design      Wire Load Model      Library
-----
SQUARER_8   4010e-3_avg                  xprim_4010e-3

Global Operating Voltage = 4.75
Power-specific unit information :
  Voltage Units = 1V
  Capacitance Units = 1.000000pf
  Time Units = 1ns
  Dynamic Power Units = 1mW {derived from V,C,T units)
  Leakage Power Units = Unitless

Cell Internal Power = 0.0000 mW {0%}
Net Switching Power = 22.6160 mW {100%}
-----
Total Dynamic Power = 22.6160 mW {100%}
Cell Leakage Power  = 0.0000


```

Example :

Multiplicand = $10001001_2 = 89_{16}$


Multiplier = $10101011_2 = AB_{16}$

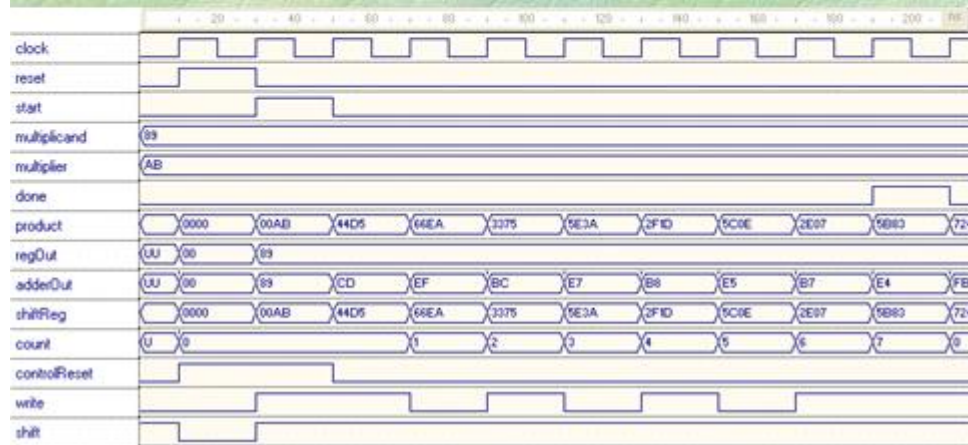Expected Result = $101101110000011_2 = 5B83_{16}$



The Design process

Verify at every step

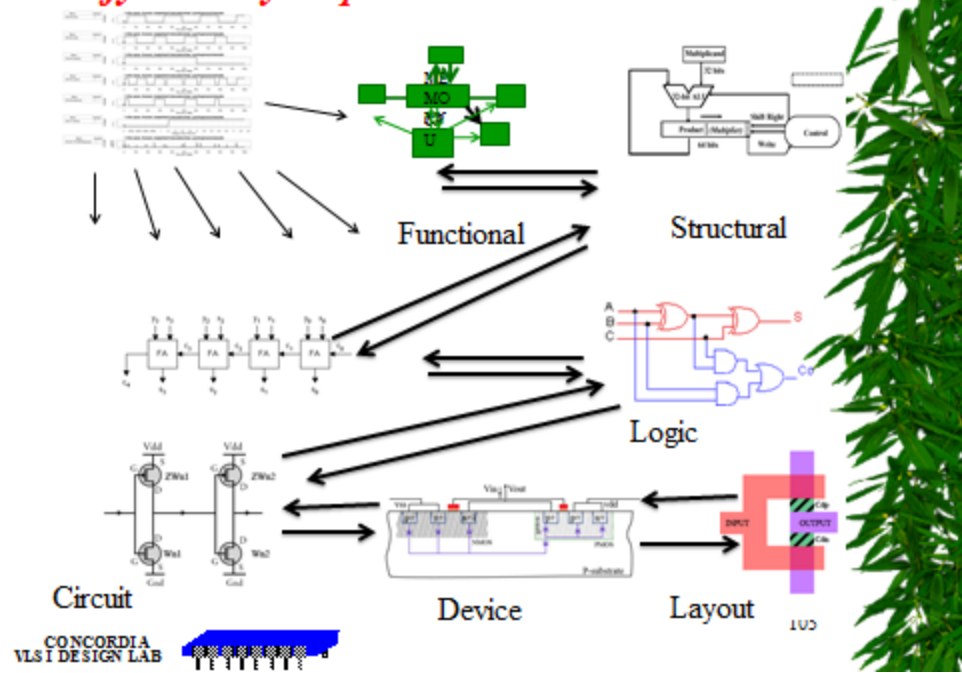

Appendix A

By: Harish Harish prepared for COEN 6501

The following Appendix, shows the design concept using VHDL in details.

VHDL DESIGN CONCEPT

The behaviour and structure of the digital circuits are described by Hardware description language which is also used to simulate the circuit and check its response. VHDL language which is a simulation and verification language is basically used as a modelling language for digital systems for many tools it is used as an intermediate form of design entry. VHDL is not case sensitive and should be saved with an extension of “.vhd”. In a VHDL language the basic building blocks is known as module which describes the corresponding hardware module. A basic module structure may include declarations, statements, tasks and functions among others. VHDL uses the ASCII character set. The lexical elements for the language include identifier and reserve words special symbols etc.

The general structure of VHDL module is an **entity** description which is followed by the description of the **architecture**. In the **entity** description the input and the output signals are declared and in the **architecture** description the internal operations of the module is specified.

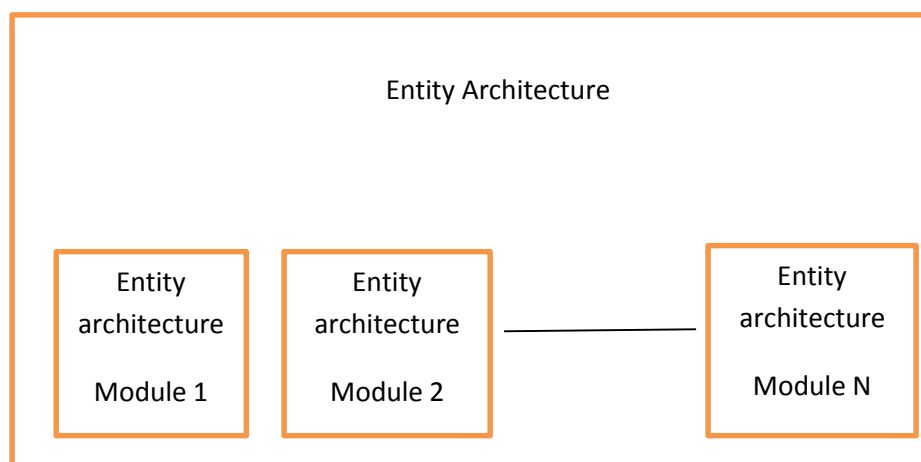


Figure 2: VHDL programme structure [1]

The name of the module is given by the **entity** declaration (here two gates with respect to the figure).the entity description of the module represents the interconnections from this module to

the external interface. The **port** declaration specifies the inputs and outputs to the module (here A, B and D are inputs signals and E is the output signal). The name of the **architecture** associated with module is given by the architecture (here it is gates). The beginning and the end of the module is represented by the concurrent statements **begin** and **end**.

 


Figure 3: VHDL module with two gates [1]

entity two_gates **is**

port (A, B, D: **in bit**; E: **out bit**);

end two_gates

architecture gates **of** two_gates **is**

signal C: **bit**;

begin

C<= A **and** B;

E<=C **or** D; ?1?

end gates;

In addition to the in and out modes two other modes are being used buffer and linkage. The inout mode and the buffer mode are similar and it is useful if the signal is really an output signal. When we want to connect a VHDL entity to a non-VHDL entity a linkage port is useful. As both of these modes involve strict restrictions these are used at a restricted level. In VHDL there are

two types of delays which can be found-**transport delays** and **inertial delays**. Inertial delay which is default delay is intended to model gates and to those devices which do not propagate short pulses from input to output. The other VHDL delay which is the transport delay is intended to model the delay introduced by the wiring, in other words it simply delays an input signal by a specified delay time. Modelling this delay can be done by simply using the keyword **transport** in the code. This simulation related delays like inertial delay can inhibit many output change.

Compilation and simulation of VHDL code

In order to verify the implement the intended design correctly and also to verify if the design meets the specification simulation of the VHDL code is necessary. Accordingly there are three phases in the simulation of the VHDL code: compilation, elaboration and simulation.

 


Figure 4: Compilation and Simulation of VHDL code [1]

The syntax of the typed VHDL source code is verified to check if it adheres to the syntax and the semantic rules by the compiler also called as the analyser. On a positive result the compiler generates an intermediate code used by the simulator. In the elaboration process the VHDL intermediate code is converted to a form used by the simulator. The simulator process consists

of an initialisation phase and actual simulation. The simulator produces the desired simulation outputs upon accepting the simulation commands. The initial value to the signal is given and the corresponding actions are scheduled by the process of scheduling a transaction. In order to facilitate the correct initialisation process an initial value can be assigned in the VHDL module. Depending upon the type of the signal some initial value is assigned in the absence of an initial value. Simulation time is set to zero and the process is executed for corresponding transactions. Basically in a simulator whenever a component changes the output is scheduled to change after specified delay. The output change is specified when the simulated time is advanced to the next time when all the input changes have been processed.

```
entity simulation_example is
```

```
end simulation_example;
```

```
architecture test1 of simulation_example is
```

```
signal A, B: bit;
```

```
begin
```

```
    P1: process (B)
```

```
    begin
```

```
        A<= '1';
```

```
        A<=transport '0' after 5 ns;
```

```
    end process P1;
```

```
    P2: process (A)
```

```
    begin
```

```
        if A='1' then B<=not B after 10ns; end if;
```

```
    end process P2;
```

```
end test1; ?1?
```

VHDL data types and operators

In VHDL there are several predefined data types which are used by the signals or they can also be user defined data type. Some of the data types are bit (0 or 1), Boolean (FALSE or TRUE), integer (in the range of $-(2^{31}-1)$ to $+(2^{31}-1)$), real (floating point number), character (any legal VHDL character), time (any integer with the units if fs, ps, ns, us, ms, sec, min, or hr). A common example of the user defined data type that is the data type created by the user is the enumeration type. In VHDL signals and variables cannot be mixed in the same assignment statement. Predefined VHDL operators are available and are grouped into seven classes- Binary logical operators, relational operators, shift operators, adding operators, unary operators, multiplying operators, miscellaneous operators. The operators in class seven gets the highest precedence when the parenthesis are not used and are applied first which is then followed by class six and then class five and so on. When operators of the same class are used they get precedence from left to right and the order of the precedence can be changed by the application of parenthesis. In the following expression

(A & not B or C ror 2 and D) = 110010

In the above relative expression, the operators are applied in the order

Not, &, ror, or, and, =

Lexical description

The VHDL text file is consisted of one or more text design files which must be prepared only from the prescribed ASCII character set.

Character set

There are various character set which are allowed in the design file. Furthermore there lot of characters which are included in the ASCII code representation to express like hexadecimal.

Lexical elements

A sequence of characters that makes up a fundamental element which cannot be divided into smaller elements is called as lexical elements. The types of lexical elements: delimiter, identifier, comment, character literal, string literal, bit string literal, abstract literal. The separators are those which are used in between first lexical elements and after the last lexical elements. Many separators can be used in between the lexical elements.

Delimiters

The character that is used in order to separate the lexical elements is called as delimiter. All statements in VHDL are terminated using a “;” character. The sequence of two delimiters is referred to as compound delimiter- =>, **,:=, /=, >=, <>, --. The use of delimiters reduces the use of specific separators in between the lexical characters.

Character literal

When a lexical element is formed by inserting one character between two apostrophe delimiter, it is known as character literal.

String literal

The lexical element formed by the insertion of sequence of graphical characters between two quotation delimiters is called a string literal. Since it is a lexical element the string literal is typed in one line. The number of characters in the sequence gives the length of the string literal.

Bit string literal

A lexical element which consists of a string of digits enclosed by the quotation character delimiters and preceded by base specifier is called as bit string literal. The base specifier is one of the letters like B-binary, O-octal, X-hexadecimal. The string of bits gives the value of a bit string literal. The association of this to a numerical value is dependent on the user.

Decimal literal

An abstract literal which is used in many high level computer languages, expressed in standard decimal notation is called as a decimal literal. The exponential part of the literal is proceeded by letter E and only real literal accept the negative exponents value.

Data types

The specifications of values the object might have and the limitation of the types of operation the object of that type needs to perform is indicated by the data type. It is named set of values. A subtype is a type along with a constraint. If it is a legitimate value for the type and if the constraint is satisfied, the value belongs to the subtype. The type from which it was constructed is called the base type of the subtype. There are two classifications- scalar and composite.

SCALAR DATA TYPES

In scalar data types, the data types have single, simple values. An integer data type may have value of 15. This includes enumeration data types, numeric data types and physical data types.

Enumeration types

An enumeration type is a scalar type in which the values are defined by simply ordering them in a list. The elements may be identifiers or character literals. The two values for type bit are 0 and 1. Built in type for Boolean includes values TRUE or FALSE and for logical operators it is *not*, *or*, *and* and *xor*. A pre-defined attribute is the one which the value function in the range is associated with. The user-defined attribute is the one in which the attribute value is defined by the user. Its general form is “attribute ATTRIBUTE_NAME:ATTRIBUTE_SUBTYPE;”

Numeric data types

Built-in numeric data types Integer and Real with its associated performance of addition, subtraction, multiplication and division are present in VHDL language. The example for pre-defined numeric data-types

Type Integer is range -----;

Type Real is range -----; ??

The ranges of the real and integer data types are implementation dependent which is in the range of -2147483647 to +2147483647. The user-defined data types are constrained numeric data types as the declaration constraints the range. The examples of user defined data types-

Type COUNTER is range 0 to 100 ??

Physical data types

A scalar numeric data type which is associated to a system of units and is used to represent entities subject to physical measurements such as time, length, voltage, current is called as physical data type. The only pre-defined data type is time which is represented as

Type TIME is range -----;

The ranges of physical data types are restricted by implementations. The declaration of any physical data type is allowed by an implementation which is in the range of -2147483647 to +2147483647. When the range is within these limits any user-defined data type may have three units as multiples of the next lower unit. Examples—

Type RESISTANCE is range 0 to Integer' high

Type POWER is range 0 to 1e19 ??

COMPOSITE DATA TYPES

The composite data types have complex values and have several components associated with it and it also represents an array of values with some relationship to one another.

Arrays

The data type in which each element has the same subtype i.e. homogeneous elements is called as an array. There are generally two predefined array types namely string and Bit_Vector. The former is used to define a character of elements and the latter is used to define an array of bits. They are-

Type string is array (positive range <>) of character;

Type Bit_Vector is array (natural range <>) of bit; ??

Here the notation $\langle \rangle$ means the range is unconstrained, which indicates the user must specify the range when declaring the object. Both string and Bit_Vector are unconstrained and the user has to specify a range n positive for sting and in natural numbers for Bit_Vector. Some of the user defined array data types

Type REGISTER_32_Bit is array (31 downto 0) of Bit;

Subtype BITVECT3 is Bit_Vector (0 to 2);

The REGISTER_32_Bit is a constrained array type which is descending in value. As the Bit vector is an unconstrained data type, subtypes with specific index ranges can be declared. BITVECT3 is a subtype of type Bit_Vector with an ascending index range 0 to 2.

Declaration of data objects

Before the referencing of the data types in assignment statement they must be declared. These declared objects are subsequently used in the further section for various other statements.

Declaration of constants

In declaration of the constants it is imperial that their values are specified. The constant name is separated from the type name by : delimiter and the type name is separated from a constant value by := delimiter. Some examples are-

Constant ALPHA_LEVEL : PROBABILITY := 0.75;

Constant INITIAL_STATE : STATE := S0;

Constant END_MARKER : Character := DEL; ??

Declaration of variables

In declaration of variable it must be seen that they are declared within a process or sub programme. The data type of the variable is specified by the variable declaration. In the declaration the values of the variables are specified if not the default value which is the left element in the type range specified in the declaration. Some examples are —

Variable STAR_COLOR, HAT_COLOR : COLOR;

Variable BETA_LEVEL : PROBABILITY := 0.0;

Variable A, B, C, D : Bit;

Variable R1, R2, R3, R4 : REG; ??

A , delimiter is used to in order to declare more than one variable of the same type. A : is used to separate the list of variable name from the data type and := is used to separate the initial value from the data type.

Declaration of signals

The signal declaration is similar to variable declaration. The signals are not be declared in processes or in sub programmes but it can be declared as ports in entity declaration or in the declarative region of architecture declarations. Some examples are ---

Signal X1, X2, X3, X4, X5: Bit;

Signal SR1, SR2, SR3, SR4: REG;

Signal DOWN_COUNT: COUNTER := COUNTER 'right; ??

VHDL libraries

The functionality of the VHDL is extended by the use of VHDL libraries and packages in defining types, functions, components and overloaded operators. Overloaded functions are generally created to handle operations involving heterogeneous data types. The package IEEE.std_logic_1164 defines a standard logic type which has nine values likewise std_logic_vectors defines logic vectors. Both the packages define overloaded arithmetic and logic operators for signed and unsigned numbers.

VHDL IMPLEMENTATION

Multiple forms of abstraction are possible. The same circuit can be implemented in different ways namely **Structural model**, **Behavioral model** and **Mixed model**. In the behavioral VHDL

description, the circuit or the system is defined at a high level of abstraction without implying any structure or technology specifying only the overall behaviour. The behavioral VHDL can also be implemented as dataflow or algorithmic level. In the data flow model data flow and control signals are specified. System working is specified in terms of data transfer between registers.

DATA FLOW IMPLEMENTATION OF FULL ADDER

architecture DATA_FLOW_IMPLEMENTATION **of** FULL_ADDER **is**

block

signal S1, S2, S3: BIT;

begin

S1 <= A **xor** B;

SUM <= S1 **xor** CIN;

S2 <= A **and** B;

S3 <= S1 **and** CIN;

COUT <= S2 **or** S3;

end block;

end DATA_FLOW_IMPLEMENTATION; ??

ALGORITHMIC IMPLEMENTATION OF FULL ADDER

architecture ALGORITHMIC_IMPLEMENTATION **of** FULL_ADDER **is**

block

begin

```

process (A,B,CIN)

variable S: BIT_VECTOR ( 1 to 3 ) := A & B & CIN;

variable COUNT: INTEGER range 0 to 3 :=0;

begin

for i:= 1 to 3 loop

  if S(i) = '1' then

    COUNT := COUNT +1;

  end if ;

end loop;

case COUNT is

  when 0 => COUNT <= '0'; SUM <= '0';

  when 1 => COUNT <= '0'; SUM <= '1';

  when 2 => COUNT <= '1'; SUM <= '0';

  when 3 => COUNT <= '1'; SUM <= '1';

end case;

end process;

end block;

end ALGORITHIC-IMPLEMENTATION; ??

```

On the other hand in the implementation of the structural model which has a low level of abstraction the components used and the interconnection between the components are clearly specified. The structural model implementations are detailed enough to specify the use of particular gates and flip-flops from specific libraries/packages.

STRUCTURAL IMPLEMENTATION OF FULL ADDER

architecture GATE_IMPLEMENTATION of FULL_ADDER is

Block

component or_gate port (A,B : in BIT; C: out BIT);

end component;

component and_gate port (A,B : in BIT; C: out BIT);

end component;

component xor_gate port (A,B : in BIT; C: out BIT);

end component;

signal S1, S2, S3: BIT;

begin

X1: xor_gate port map (A, B, S1);

X2: xor_gate port map (S1, CIN, SUM);

A1: and_gate port map (CIN, S1, S2);

A2: and_2 port map (A, B, S3);

O1: or_gate port map (S2, S3, COUT);

end Block;

end GATE_IMPLEMENTATION ; ??

Behavioral and structural design techniques are often combined giving rise to mixed VHDL implementation. Here different techniques are used to design different parts of the module. The automation tools generate efficient hardware hence they designed using behavioral level. Manual

optimisation needed by the memory structures are done through structural design as opposed to the behavioral modelling.

MIXED IMPLEMENTATION OF FULL ADDER

architecture MIXED_IMPLEMENTATION **of** FULL_ADDER **is**

signal WIRE: BIT;

component XOR_G

port (X1, X2: **in** BIT; XO1: **out** BIT);

end component;

for all: XOR_G **use** XOR_GATE(BEHAVIORAL);

begin

XOR1: XOR_G **port map** (X,Y,WIRE);

XOR2: XOR_G **port map** (WIRE,CIN,SUM);

COUT <= (WIRE **and** CIN) **or** (X **and** Y);

end MIXED_IMPLEMENTATION ?3?

SEQUENTIAL CIRCUITS AND VHDL IMPLEMENTATION

A combinational circuit is the one which produces its output based on the current inputs while a sequential circuit generates the outputs based on the current inputs and the previous states, which imply that memory, latches and flip-flops are common sequential circuits. The sequential logic responds to changes dependent on the clock. The primitives are required to model selective activity conditional on clock, edge triggered devices, sequences of operation in the process of modelling sequential circuits.

Shift register

A shift register shifts the data either to the left or to the right through a number of cascaded flip-flops. The VHDL code shows the shift register with a shift right function through eight flip-flops. In the code the lines 13 and 14 asynchronously resets the flip-flops while lines 15 and 16 shift right the flip-flop when rising edge of the clock CLK occurs. Line 19 gives the SO output directly to FF8.

```
library IEEE;

use IEEE.std_logic_1164.all;

entity SHIFTR is

port (CLK, RSTn, SI: in std_logic; SO: out std_logic);

end SHIFTR;

architecture RTL of SHIFTR is

signal FF8: std_logic_vector (7 downto 0);

begin

posedge: process (RSTn, CLK)

begin

if (RSTn, CLK)

begin

if (RSTn ='0') then

FF8<= (FF8 'range =>'0');

elseif (CLK'event and CLK ='1') then

FF8 <=SI&FF8 (FF8'length-1 downto 1);
```

```

end if;

end process;

SO <= FF8 (0);

end RTL; ??

```

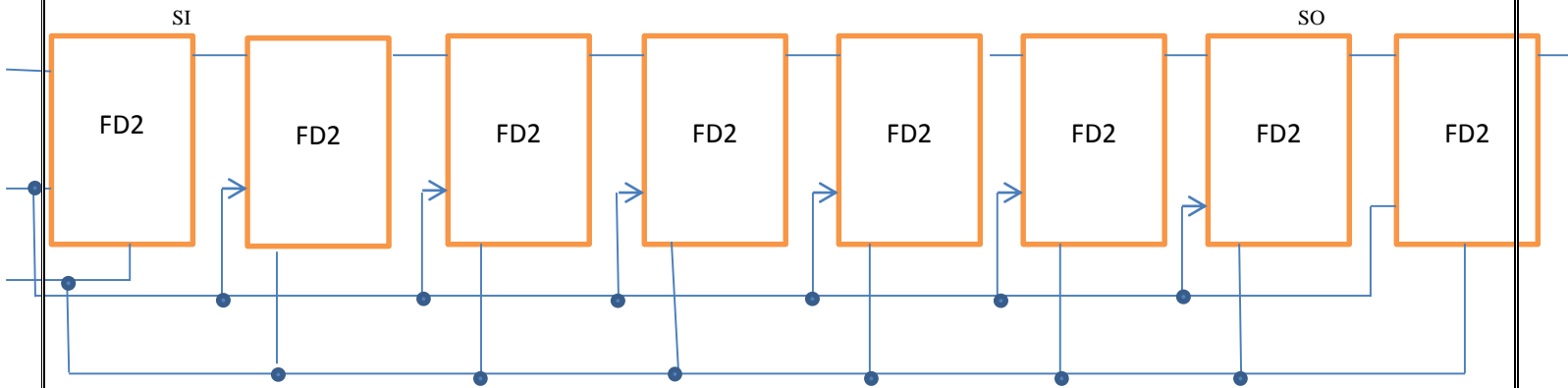


Figure 5: Synthesised schematic for shifter [2]

COMBINATIONAL CIRCUITS AND VHDL IMPLEMENTATION

The combinational circuits can be modelled by the VHDL by the use of concurrent statements. These concurrent statements are those which are ready to be executed and which get evaluated any time and also every time when the signal on the right side of the statement changes. VHDL assignment statements can be given as an example for concurrent statements. The right side of the concurrent statement is monitored by the VHDL simulator and when the signal changes the right side expression is immediately re-evaluated. After an appropriate delay the new value is assigned to the left side of the signal. The location of this concurrent statement in the programme is not important.

Encoder

An encoder converts one form of input pattern to a required form of output pattern. Here the encoder has a 4-bit input SEL and a 16-bit output Y. All the bits in the output will be 1, except the value represented by SEL. In the first VHDL code the programme uses if statement inside the process statement with the input SEL as process sensitivity list.

```

library IEEE;

use IEEE.std_logic_1164.all;

use IEEE.std_logic_unsigned.all;

entity ENCODER is

port (SEL: in std_logic_vector (0 downto 0) ;Y: out std_logic_vector (15 downto 0)) ;

end ENCODER;

architecture RTL of ENCODER is

begin

P0: process (SEL)

begin

Y <= (Y'range => '1');

if (SEL="0000") then

Y (0) <= '0';

elseif (SEL="0001") then

Y (1) <= '0';

elseif (SEL="0010") then

Y (2) <= '0';

elseif (SEL="0011") then

Y (3) <= '0';

elseif (SEL="0100") then

Y (4) <= '0';

```


elseif (SEL="0101") then

Y (5) <='0';

elseif (SEL="0110") then

Y (6) <='0';

elseif (SEL="0111") then

Y (7) <='0';

elseif (SEL="1000") then

Y (8) <='0';

elseif (SEL="1001") then

Y (9) <='0';

elseif (SEL="1010") then

Y (10) <='0';

elseif (SEL="1011") then

Y (11) <='0';

elseif (SEL="1100") then

Y (12) <='0';

elseif (SEL="1101") then

Y (13) <='0';

elseif (SEL="1110") then

Y (14) <='0';

else

```
Y (51) <='0';
```

```
end if;
```

```
end process;
```

```
end RTL;
```

This coding uses a process statement and it includes conv_integer from the package IEEE std_logic_unsigned.

architecture RTL of ENCODER is

```
begin
```

```
P3: process (SEL)
```

```
begin
```

```
Y <= (Y'range => '1');
```

```
Y (conv_integer (SEL)) <= '0';
```

```
end process;
```

```
end RTL; ?4?
```

PROGRAMMABLE LOGIC DEVICES

Programmable logic devices helps in the removal of multiple off-the shelf devices and the inconvenience associated external wires. These devices allow an easy reprogramming and it is easier to change the design in case of error. They basically contain an array of basic building blocks that can be used to implement whatever functionality one desires. They differ in the building blocks or the amount of programmability they provide.

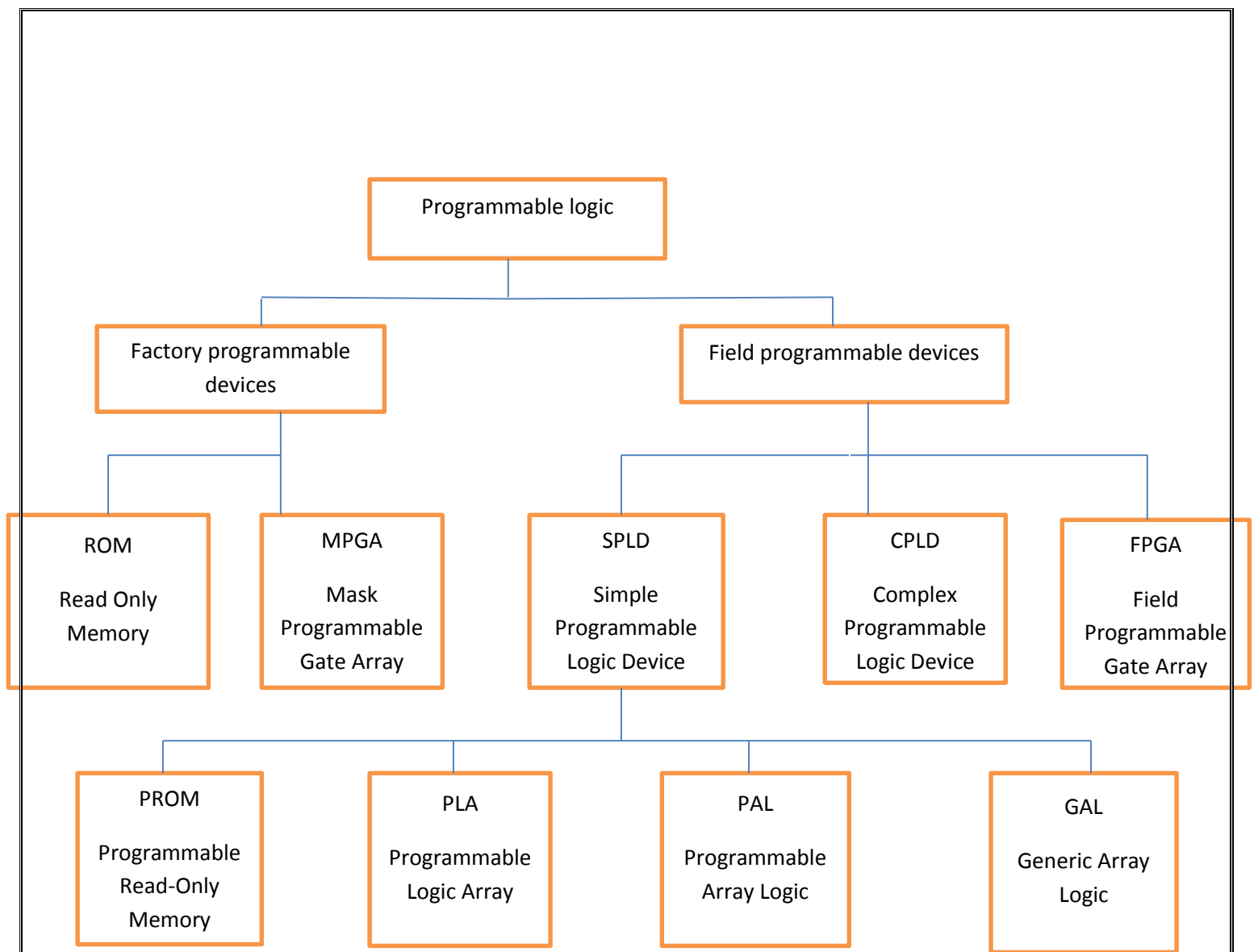


Figure 6: Major programmable logic devices [1]

The field programmable logic devices are used in the programmer's user's field rather than a semi-conductor fab while the field programmable devices are programmed in a factory to meet the customers' requirements. PAL's and PLA's contain arrays of gates allowing users to implement combinational function in two levels of gates. The special case of PLA is PAL wherein OR array is fixed and only AND array is programmable. They also may contain flip-flops. The use of random access memory in Xilinx led to the creation of FPGA that integrate fairly a large amount of logic.

Simple programmable logic devices

The early generation of programmable logic devices is collectively called simple programmable logic device.

Read-Only Memory

The read-only memory is built up of an array of semiconductor devices that are interconnected enabling it to store a binary data. The data that is stored in ROM is permanent and can be read out whenever wanted, but it cannot be changed under normal operating conditions. A ROM consists of a decoder and a memory array. When a pattern of n 1's and 0's are applied to the input the output obtained is exactly 2^n decoder output which is 1. In the memory the decoder output line selects one of the words and the bit pattern stored in the word is transferred to the memory output lines. Basically there many types of ROM namely- user programmable ROM's, erasable programmable ROM's, electrically erasable and programmable ROM's and flash memory.

Programmable Logic Array

A programmable logic array performs the same basic function as a ROM. An n input and n output PLA can realise m functions of n -variables. Basically the internal organisation of a PLA is different from that of ROM. In PLA the decoder is replaced with an AND array which is used to realise the selected product terms of the input variables. Meanwhile the OR array OR's the product terms together which is needed to form the output functions. The PLA may use NOR-NOR logic instead of AND-OR logic.

Programmable Array Logic

The PAL is a special case of programmable logic array in which the AND array is programmable and OR array is fixed. Structurally the PLA and the PAL resemble one another but PAL is less expensive than PLA as only the AND gate is programmable. In a PAL a buffer is used as each input has to drive many AND gate inputs. In order to make the desired connections to the AND gate inputs some of the interconnection points are programmed while programming the PAL. Unlike the general PLA each function must be realised and simplified by itself without regard to common terms as the AND gates cannot be shared with two or more OR gates.

Programmable Logic Devices

With the improvement in the integrated technology the PAL's are enabled to be reprogrammable now called as PLD's. In addition to the AND –OR arrays that the PAL's have the PLD's contains some multiplexers and some additional programmability and these are named with respect to their input and output capability. Typically the PLD's have some 8 to 12 I/O pins. Further each output pin is connected to an output macrocell which has a D-flip flop connected to it. The programmable I/O pins can act as inputs or combinational or flip-flop outputs. One can find dedicated output clocks in some PLD's while others have a dual-purpose pin which can be used either as a clock or as an input. Tristate buffers are present in all the PLD's at the output. PALASM and ABEL are the two programming languages used in PAL's and PLD's.

Complex programmable logic devices

The developments in the IC technology have made it possible to create programmable ICs equal to several PLDs in the same chip referred to as complex programmable logic devices (CPLDs). When these are incorporated with storage elements digital systems are created in the IC. Basically a CPLD is an IC consisting of a number of PAL- like logic blocks together with a programmable interconnect matrix. The PLD are necessarily interconnected using a crossbar-like switch typically consisting of 500 to 10,000 logic gates. These CPLDs are electronically erasable and reprogrammable and hence called as EPLDs. There are number of macrocells that are present in a typical CPLD. An interconnection array is used to establish the connection between the function blocks. Each macrocell consists of a flip-flop and an OR gate that has its input connected to an AND gate array. Those CPLDs which are based on PALs has each OR gate which is associated with fixed set of AND gates and those CPLDs based on PLAs has AND gate output connected to any OR gate input in that block.

The signal generated in functional block (PLA) is routed through a macrocell to an I/O pin. Any of the 36 inputs of the IA can be connected to any of the inputs of the 48 AND gates. Each OR gate has to accept upto 48 product term input from the AND array. The mux1 is programmed to select the OR gate output while the mux2 can be programmed to select their combinational output or flip-flop output. The output is fed to the interconnect array and to output cell which

includes the three-state buffer to drive the I/O pin. When the I/O is used as an input, the buffer must be disabled.

Field programmable gate arrays

FPGAs are ICs which contain an array of identical logic blocks that are provided with programmable interconnections. There are number of FPGA products available namely Xilinx, Altera, lattice, actel, cypress. Arrays of programmable logic blocks are distributed within the FPGA surrounded by input/output interface blocks. Basically there many types of programming blocks like multiplexers and logic gates on one hand while some use only transistors. The architecture also differs according to the use and purpose. The programmable blocks like logic block, interconnect help to re-programme FPGA. In FPGA them interconnect can be programmed to make or break connection. There might be different interconnects used depending upon the FPGA company like general purpose interconnect, direct interconnect, global lines and so on. StaticRAM programming technology, EPROM/EEPROM/flash programming technology, Antifuse programming technology are the programming technologies used to programme FPGA. In more recent times the vendors have incorporated embedded processors, dedicated multipliers, analog-to-digital converters and so on in FPGAs.

VHDL SYNTHESIS ENVIRONMENT

Designer analyser. The design analyser is a user interface tool which has a command window for the users in order to supply synthesis commands.

VHDL compiler. The compiler parses VHDL code, checks for syntax errors and checks for VHDL construct in the code that are synthesizable. It also generates a summary report on the components used.

Design compiler. The design is optimised by the design compiler based on the synthesis constraints such as speed and area requirements.

Design time. The design time is a timing analyser which is used to find the critical path and to perform timing checks.

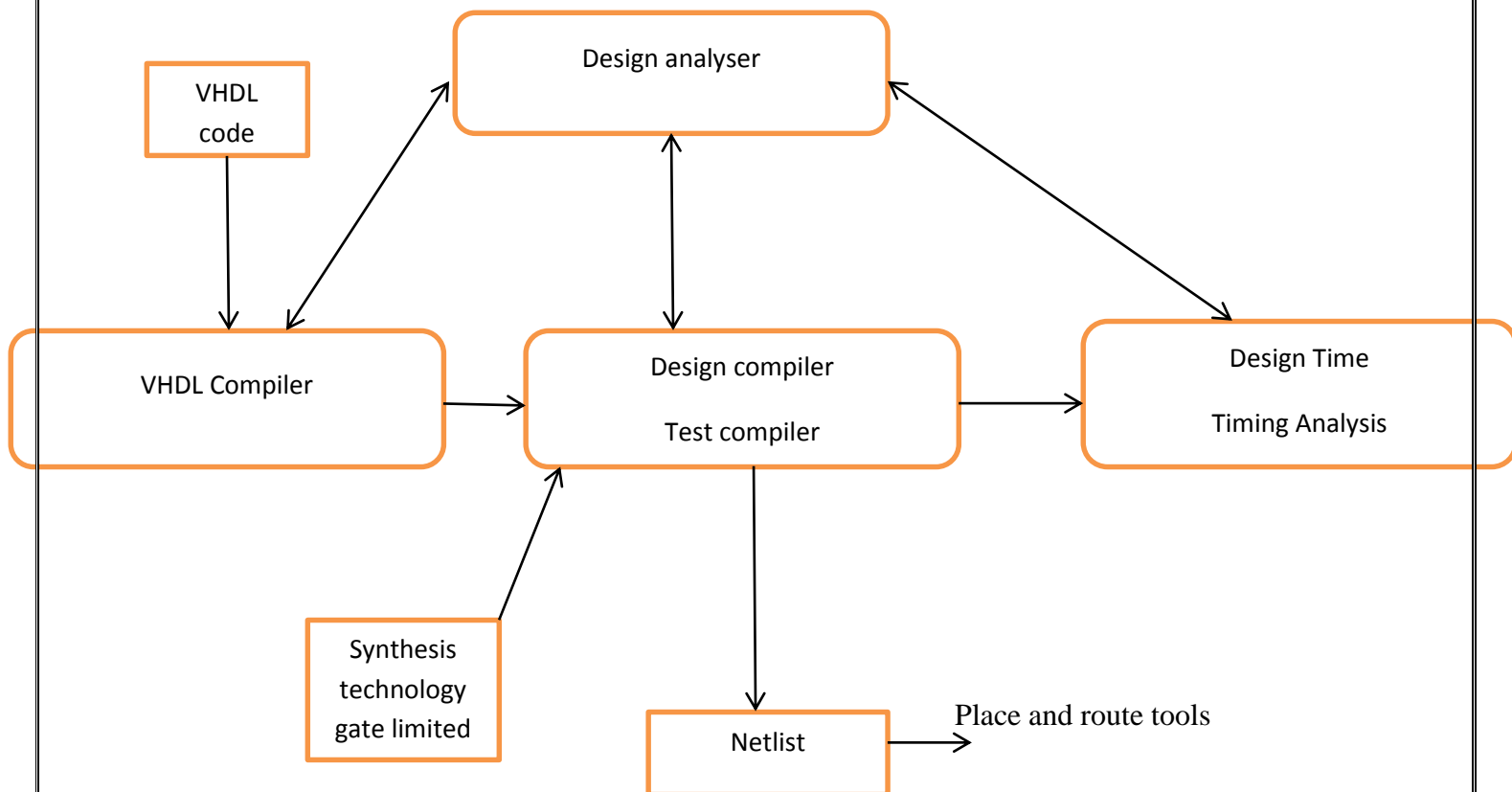


Figure 7: Synopsys synthesis tools [2]

There are many commands in the directory for synthesis. Directory syn is used to run the synthesis, unix command design_analyser is used to bring synopsys design analyser. This also executes commands specified in the file .synopsys_dc.setup, and brings up the design window. The synthesis script file compile.report generates synthesis results to be placed in the REPORT directory. When both synopsys VHDL and synthesis tools use the same library there would be a time stamp delay so it is better to separate both the libraries.

A synthesis technology library consists of definitions of basic components, operating conditions and wire load models. Each component consists of its own logical function, timing, input pin loading and output pin drive information. The synthesis usually uses library_name.sdb. The command read/acct/synlib/Isi/lca300k.db can be used to read the synthesis technology inside the designer analyser. It is important that we select a good synthesis library to match design objectives such as speed requirements, cost, production schedule, and design tools.

REFERENCES

1. INTRODUCTION TO DIGITAL SYSTEMS: Modeling, Synthesis, and Simulation Using VHDL Mohammed Ferdjallah
2. Digital systems design using VHDL Charles H.Roth, Lizy Kurian John
3. Digital systems design and VHDL synthesis K.C.Chang
4. Prof. A.Alkhalili Notes
5. Verilog HDL: A Guide to Digital Design and Synthesis, Second Edition Samir Palnitkar
6. VHDL Design Representation and Synthesis, Second Edition James R. Armstrong, F. Gail Grey

Figures

[1] Digital systems design using VHDL Charles H.Roth, Lizy Kurian John

[2] Digital systems design and VHDL synthesis K.C.Chang

Examples and VHDL codes

?1? Digital systems design using VHDL Charles H.Roth, Lizy Kurian John

?2? VHDL Design Representation and Synthesis, Second Edition James R. Armstrong, F. Gail

?3? Prof. A.Alkhalili Notes

?4? Digital systems design and VHDL synthesis K.C.Chang

 


Fig. 1 Design Concept using VHDL